

## Experiment 7

**Aim:** To design and simulate 4-bit BCD adder.

**Tools Used:** Circuit Verse.

**Theory:** BCD is Binary Coded Decimal number, where each digit of a decimal number is respected by its equivalent binary number. That means, LSB of a decimal number is represented by its equivalent binary number and similarly other higher significant bits of decimal number are also represented by their equivalent binary numbers.

Suppose, we have 4 bit numbers i.e. A and B which can vary from 0 (0000) to 9 (1001 in binary). For example:

Example 1:

```
Input :  
A = 0111  B = 1000  
Output :  
Y = 1 0101  
  
Explanation: We are adding A(=7) and B(=8).  
The value of binary sum will be 1111(=15).  
But, the BCD sum will be 1 0101,  
where 1 is 0001 in binary and 5 is 0101 in binary.
```

Example 2:

```
Input :  
A = 0101  B = 1001  
Output :  
Y = 1 0100  
  
Explanation: We are adding A(=5) and B(=9).  
The value of binary sum will be 1110(=14).  
But, the BCD sum will be 1 0100,  
where 1 is 0001 in binary and 4 is 0100 in binary.
```

If the decimal numbers are less than or equal to 9, then the value of BCD sum and the binary sum will be same otherwise they will be diff by 6 (0110 in binary).

Decimal	Binary Sum					BCD Sum				
	C'	S3'	S2'	S1'	S0'	C	S3	S2	S1	S0
0	0	0	0	0	0	0	0	0	0	0
1	0	0	0	0	1	0	0	0	0	1
2	0	0	0	1	0	0	0	0	1	0
3	0	0	0	1	1	0	0	0	1	1

4	0	0	1	0	0	0	0	1	0	0
5	0	0	1	0	1	0	0	1	0	1
6	0	0	1	1	0	0	0	1	1	0
7	0	0	1	1	1	0	0	1	1	1
8	0	1	0	0	0	0	1	0	0	0
9	0	1	0	0	1	0	1	0	0	1
10	0	1	0	1	0	1	0	0	0	0
11	0	1	0	1	1	1	0	0	0	1
12	0	1	1	0	0	1	0	0	1	0
13	0	1	1	0	1	1	0	0	1	1
14	0	1	1	1	0	1	0	1	0	0
15	0	1	1	1	1	1	0	1	0	1
16	1	0	0	0	0	1	0	1	1	0
17	1	0	0	0	1	1	0	1	1	1
18	1	0	0	1	0	1	1	0	0	0
19	1	0	0	1	1	1	1	0	0	1

Table 1: Truth Table of Binary to BCD Adder.


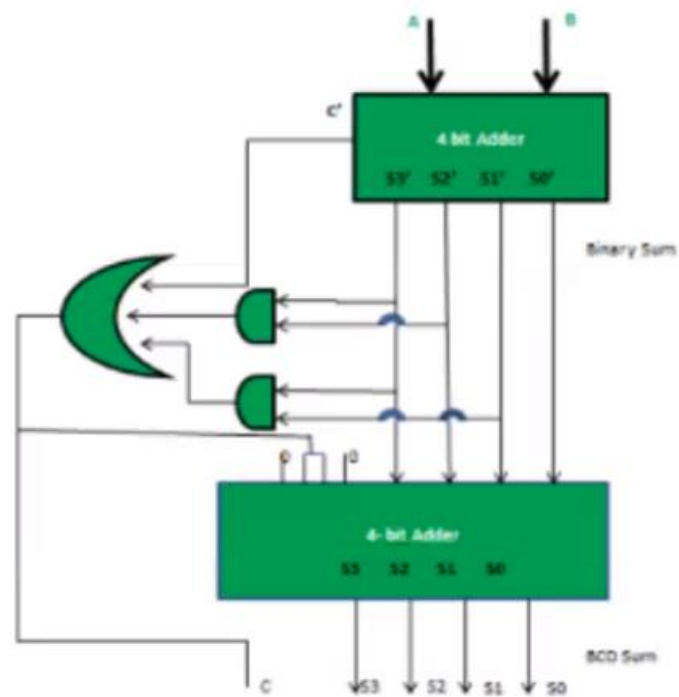



Fig 1: Blueprint of 3 Bit Binary to BCD Adder.
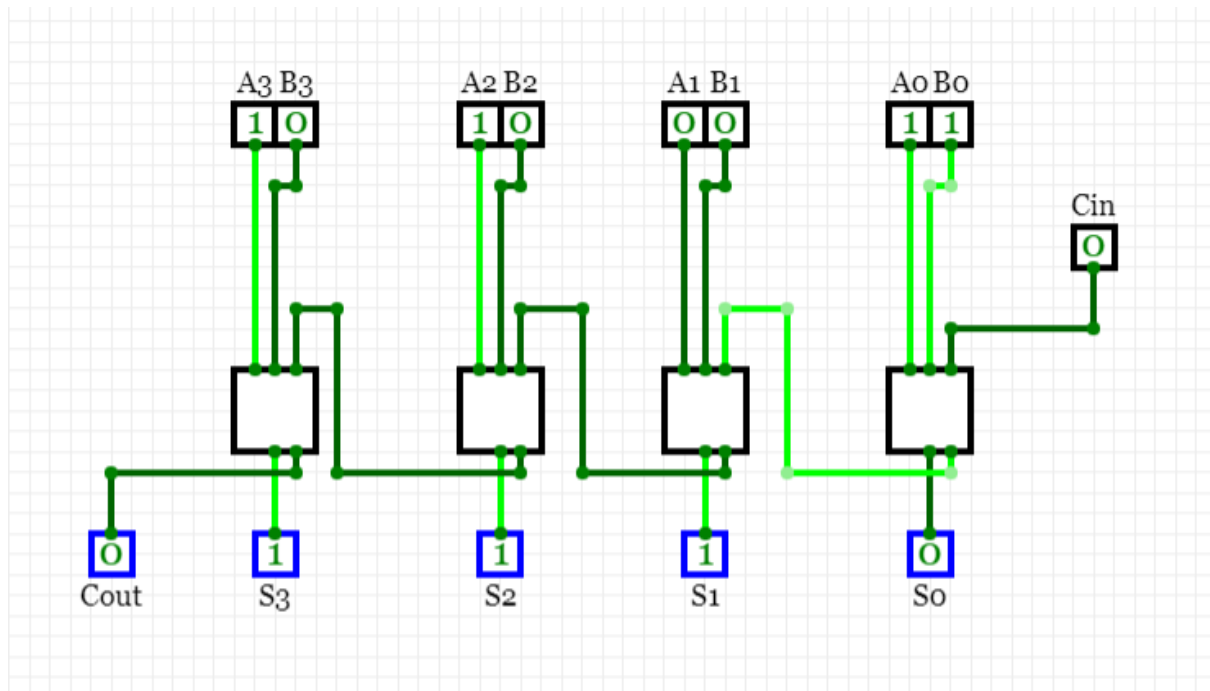
## Observations:

Circuit Representation of Full Adder Circuit:



Circuit Representation of Binary to BCD:

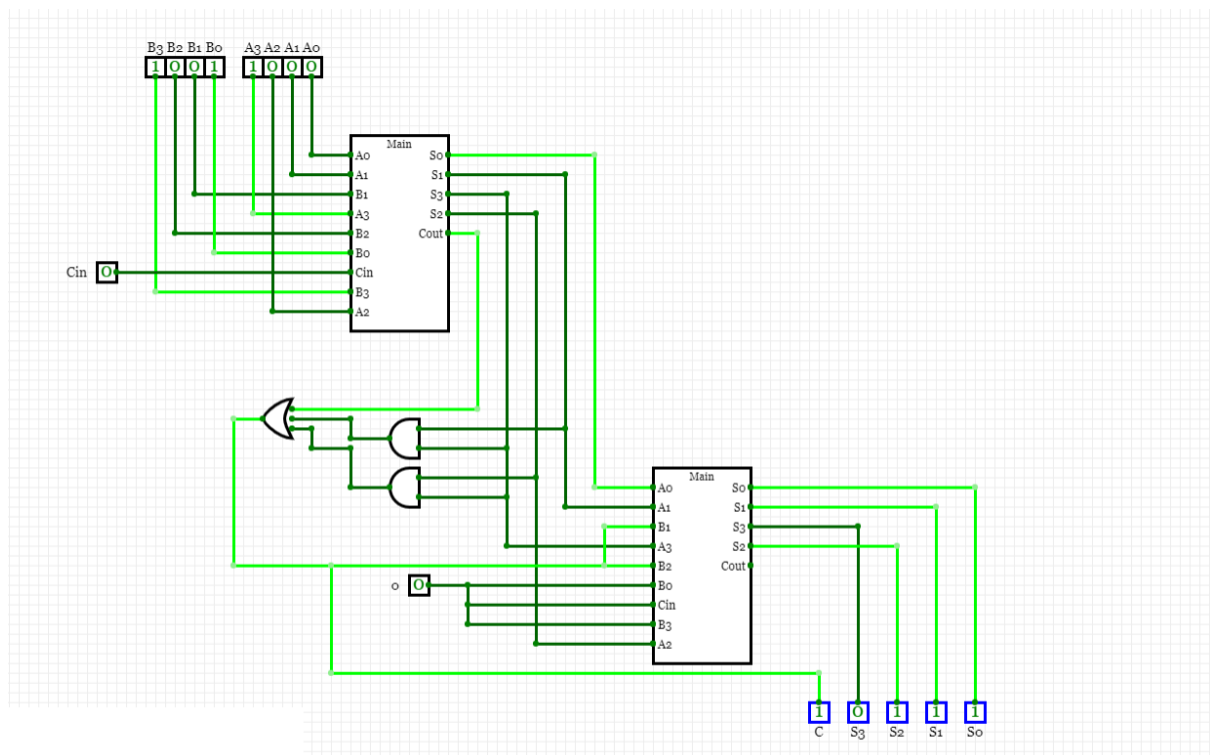

**Result:** The designing and simulation of binary to BCD adder has been done successfully.

<b>CRITERIA</b>	<b>TOTAL MARKS</b>	<b>MARKS OBTAINED</b>	<b>COMMENTS</b>
<b>(A) CONCEPT</b>	<b>2</b>		
<b>(B) IMPLEMENTATION</b>	<b>2</b>		
<b>(C) PERFORMANCE</b>	<b>2</b>		
<b>TOTAL</b>	<b>6</b>		